

Question Bank (G scheme)

Name of subject: Electrical Technology

Subject code : 17331

Semester : III

Unit Test: II

Course : CM/IF3G

CHAPTER 3 AC SERIES CIRCUITS (10 marks for 2nd t half part)

3 marks

- 1) Draw circuit diagram for measurement of single phase power using dynamometer type wattmeter.
- 2) State types of power. Give their expressions and show them on power triangle.

4marks

- 3) A resistance of 5Ω , inductance of $10\mu\text{H}$ and capacitance of $100\mu\text{F}$ are connected in series across 230V, 50Hz ac supply. Calculate
 - a. inductive reactance
 - b. capacitive reactance
 - c. impedance
 - d. current
- 4) A circuit draws a current of 10A at a voltage of 200 V and its power factor is 0.8 lagging. Calculate:
 - a. Active power
 - b. Reactive power
 - c. Apparent power.
 - d. Also draw the power triangle.

CHAPTER 4 THREE PHASE CIRCUITS (14 marks)

3 marks

- 5) Draw a neat labeled sketch of three phase balanced star connected and delta connected systems, mark all line and phase voltages.
- 6) State relation between phase current and line current, phase voltage and line voltage for following systems:
 - a. Star connected balanced system
 - b. Delta connected balanced system.

4 marks

- 7) A three-phase 400 V, 50Hz, a.c. supply is feeding a three phase delta connected load with each phase having a resistance of 25 ohms, an inductance of 0.15H and capacitance of 120 microfarads in series. Determine the line current and total three phase power absorbed.
- 8) Draw three phase AC wave form. Define phase sequence and balanced load for the three phase AC.
- 9) State advantages of three phase circuits over single phase circuits.
- 10) Three identical coils, each of $(4.2 + j5.6)$ ohms are connected in star across 415 V, 3-phase, 50Hz supply. Calculate:
 - a. phase voltage
 - b. phase current
 - c. power factor
 - d. power absorbed by each phase.
- 11) Compare 3 phase Star connection with 3 phase Delta connection.

CHAPTER 5 ELECTRICAL MACHINES (20marks)

3Marks

- 12) Define efficiency and voltage regulation of single phase transformer.
- 13) Give one application of the following single phase motors:
 - a. Resistance split phase motor
 - b. Capacitor start motor.
 - c. Universal Motor
- 14) Compare core type and shell type transformer on any three points

4 Marks

- 15) Give principle of operation and working of capacitor start single phase induction motor.
- 16) Give construction and working principle of single phase transformer.
- 17) Give principle of operation and working of universal motor.
- 18) Compare auto transformer with two winding transformer.

19) Explain principle of operation of single phase induction motor.

CHAPTER 6 ELECTRICAL SAFETY (8 marks)

3 Marks

- 20) Draw a neat labeled diagram of pipe earthing.
- 21) Give classifications of fuses.
- 22) State any four precautions to be taken against electric shock
- 23) State need of earthing.

4 Marks

- 24) What is fuse? Also explain the working of HRC fuse in brief..
- 25) State the factors on which severity of electric shock depends.