

# Question Bank 2(I-Scheme)

Name of course: Basic Electronics

Unit Test: II

Subject code: 22225 (BEC)

Semester: II

Program: CM/IF

## Chapter: 3 Bipolar Junction Transistors

### 2 mark questions:

- 1) Define Transistor & Draw symbol of NPN Transistor.
- 2) Draw the construction of NPN Transistor.
- 3) Define: a) Current gain(  $\alpha$  ) b) Current gain(  $\beta$  )
- 4) Draw the output characteristics of Transistor in CE mode.
- 5) Define DC load line & Operating point.
- 6) State need of biasing.
- 7) State the advantages of voltage divider biasing over base bias.
- 8) State the applications of RC coupled CE amplifier.

### 4 mark Questions

- 1) Explain working principle of NPN Transistor.
- 2) Derive the relationship between  $\alpha$  &  $\beta$  of transistor.
- 3) Draw & explain voltage divider biasing.
- 4) Compare CB & CE configuration of transistor.
- 5) If  $\alpha$  of a transistor is 0.9, calculate  $\beta$ .
- 6) If  $\beta$  of a transistor is 98,  $I_c = 4.5\text{mA}$ , then calculate base current.
- 7) State the significance of operating point in Transistor biasing.
- 8) Explain how transistor can be used as switch.
- 9) Draw & explain single stage CE amplifier.
- 10) In a voltage divider biasing ckt,  $V_{cc} = 10\text{V}$ ,  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 5\text{k}\Omega$ , &  $R_E = 100\Omega$ ,  $R_C = 1\text{k}\Omega$ , calculate  $I_c$  &  $V_{ce}$ .  
(Consider  $\beta = 100$ ,  $V_{be} = 0.7\text{V}$ )

## Chapter: 4 (FIELD EFFECT TRANSISTOR)

### 2 mark questions:

- 1) State different types of FET.
- 2) Draw the symbol of N-channel & P-channel JFETs.
- 3) Draw the symbol of Depletion type & Enhancement type MOSFET.
- 4) State the application of JFET.

5) State the application of MOSFET.

**4 mark questions:**

- 1) Compare FET& BJT.
- 2) Draw & Explain N-channel JFET construction.
- 3) Draw & Explain P-channel JFET construction.
- 4) Explain Working Principle of N-channel JFET.
- 5) Draw & Explain Transfer characteristics of JFET.
- 6) Define following terms:
  - a) Dynamic Drain Resistance
  - b) Amplification Factor
  - c) Transconductance
  - d) Pinched off voltage
- 7) Explain Working Principle of Depletion type MOSFET (n-channel).
- 8) Explain Working Principle of Enhancement type MOSFET (n-channel).

## **Chapter: 5 Transducers and Sensors**

### **2 Marks questions**

- 1) Define Transducer. Give its two applications.
- 2) Define active and passive transducers.
- 3) Give two applications of Transducer.
- 4) State advantages of electrical transducer.
- 5) List application of photo-transistor transducer.
- 6) Define piezo-electric effect.

### **4 Marks Questions**

- 1) Explain selection Criteria for Transducer.
- 2) Explain Resistive Transducer With an example.
- 3) Explain Inductive Transducer With an example.
- 4) Describe construction and working principle of strain gauge.
- 5) Describe construction and working principle of L.V.D.T.
- 6) Write procedure to measure temperature using thermocouple
- 7) Describe construction of photo diode transistor

