

**BHARATI VIDYAPEETH INSTITUTE OF
TECHNOLOGY**

QUESTION BANK

Unit Test-II (Shift:-I & II)

Program: - ME3I

Semester: - III

Course:- BASIC ELECTRICAL & ELECTRONICS ENGINEERING(22310)

CHAPTER 9 BIPOLAR JUNCTION TRANSISTOR

Question For 2 Marks

- 1) Draw the symbols & label the terminals of : a) NPN transistor. b) PNP transistor.
- 2) State input & output terminals in CB & CE configuration of BJT.
- 3) Draw symbol & label the terminals of : a) FET. b) BJT.
- 4) State different biasing conditions of BJT.
- 5) Define alpha & beta of transistor.

Question For 4 Marks

- 1) Draw & explain the transistor as a switch.
- 2) Draw the symbol of PNP transistor & explain its working.
- 3) Compare CB & CE configuration for BJT.
- 4) Define alpha & beta of transistor. State relationship between them.
- 5) Describe the working of transistor (BJT) as an amplifier.
- 6) Explain thermal runaway.
- 7) Explain the working of CE configuration.

CHAPTER 8 DIODE CIRCUITS & REGULATED POWER SUPPLY

Question For 2 Marks

- 1) Define rectifier.
- 2) What is rectifier. How are they classified?
- 3) Define ripple factor & efficiency.
- 4) Define load regulation. Give formula.
- 5) Name the different types of filters used in rectifier.

Question For 4 Marks

- 1) Draw the circuit diagram & explain the working of half wave rectifier.
- 2) Draw the circuit diagram & explain the working of full wave rectifier.
- 3) Draw the circuit diagram & explain the working of bridge wave rectifier.
- 4) Compare half, full & bridge wave rectifier.(4 points)
- 5) Draw block diagram of regulated power supply. State function of each block.
- 6) Draw LC filter with full wave rectifier. Also draw its waveform.
- 7) Draw CLC filter with full wave rectifier. Also draw its waveform .
- 8) Draw L filter with full wave rectifier. Also draw its waveform.
- 9) Draw C filter with full wave rectifier. Also draw its waveform.
- 10) Define load regulation & line regulation.

CHAPTER 7 SEMICONDUCTOR DIODE

Question For 2 Marks

- 1) Draw symbols of LDR & DIODE.
- 2) Draw symbols of Zener diode & UJT
- 3) List specifications of diode.
- 4) State applications of a PN junction diode.
- 5) State applications of a Zener diode.

Question For 4 Marks

- 1) State working principle of LED. Give two applications.
- 2) Draw & explain the characteristics of Zener diode with circuit diagram.
- 3) Explain avalanche breakdown of PN junction.
- 4) Explain the term potential barrier & depletion region in case of PN junction diode.
- 5) Sketch V-I characteristics PN Junction diode.

CHAPTER 6 ELECTRONIC COMPONENTS & SIGNALS

Question For 2 Marks

- 1) List types of fixed resistors.
- 2) List types of variable resistors.
- 3) List types of fixed capacitor.
- 4) List application of variable capacitor.
- 5) Define inductance.

Question For 4 Marks

- 1) Explain the color code for resistance value.
- 2) List specifications for capacitor.
- 3) Draw & explain the construction of air core inductor.
- 4) What is active & passive components.
- 5) Define the following term related with an AC quantity:
 - a) Waveform b) Frequency
 - c) Amplitude d) Time period
