

Question Bank (G Scheme)

Name Of Subject: VLS

Unit Test:

I

Subject Code: 17659

Course:

EJ6G

Semester: VI

Chapter 1: Introduction TO Advanced Digital Designs

14 M

3 Marks

1) Define:

a) Metastability

b) Noise

Margin

c) Power Fan-Out

d) Skew

2) Comparison between Melay & Moore machines.

4 Marks

3) Differentiate between asynchronous sequential and synchronous sequential circuits.

4) Draw & explain Melay machines.

- 5) Draw & explain Moore machines.
- 6) Draw state diagram & block diagram of Mealy state machine with clocked output.
- 7) Draw state diagram & block diagram of Moore state machine with clocked output.
- 8) Explain 3-bit asynchronous down counter.

Chapter 2: Introduction TO CMOS technology

20M

3 Marks

- 9) State the important application of VLSI.
- 10) List the basics IC fabrication process.
- 11) Write short note on n-well fabrication process of CMOS.
- 12) Write short note on twin-tube fabrication process of CMOS.
- 13) Explain operation of CMOS inverter.

4 Marks

- 14) Comparison between BJT & CMOS.
- 15) Describe how silicon wafer is prepared.
- 16) Explain the process of epitaxial growth of process.

- 17) Describe the process of Ion implantation for fabrication of IC.
- 18) Explain the Oxidation process for fabrication of IC
- 19) Explain how integrated resistor is fabricated.
- 20) Explain how integrated capacitor is fabricated.
- 21) Explain operation of CMOS NOR gate
- 22) Explain operation of CMOS NAND gate.
- 23) Design a logic circuit for $Z = \overline{AB + CD}$ using CMOS NAND gate.

Chapter 3: Introduction to VHDL

6M

3 Marks

- 24) What is VHDL & give the history of VHDL.

4 Marks

- 25) What are the Pros & Cons of VHDL.