

Question Bank (G scheme)

Name of subject: ELECTRONICS DEVICES AND CIRCUITS

Subject code: 17319

Semester: III

Unit Test :II

Course : EJ/IS/IE

Chap 3. Amplifiers (4 marks)

4 marks question

- 1) Draw circuit diagram of single tuned amplifier with frequency response curve.
- 2) Draw & explain double tuned amplifier with its frequency response

Chapter.4 Feedback Amplifiers & Oscillators (12 marks)

3 marks

- 3) Explain the advantages and disadvantages of negative feedback.
- 4) Draw the ckt. Diagram of crystal oscillator. Give the basic principle
- 5) A phase shift oscillator has $R=220\text{Kohms}$, $C=500\text{pF}$. Calculate the frequency of oscillation.

4 marks

- 6) Draw the block diagram and circuit diagram for current series feedback amplifier.
- 7) Explain the effect of negative feedback on voltage gain, input & output resistances, distortion, bandwidth and noise of piezoelectric crystal and also give the equivalent ckt. Diagram.
- 8) Draw & explain RC phase shift oscillator.
- 9) Explain the advantages and disadvantages of crystal oscillator.

Chapter.5 Time Base Generators (12 marks)

3marks

- 10) Explain operation of UJT with neat diagram.
- 11) Give application of sweep generators in TV and CRO.
- 12) Draw & explain UJT relaxation oscillator. Draw the waveforms & write the formula of frequency.

4 marks

- 13) Draw and explain the operation of Bootstrap sweep circuit.
- 14) Explain construction of UJT and draw its symbol.
- 15) Draw and explain the operation of Miller sweep circuit.
- 16) Draw and explain the operation of current time base generator.
- 17) Give applications of UJT.
- 18) A UJT with $\eta=0.62$ is used in a relaxation oscillator circuit with

19) $R=5k\Omega$ and $C=0.05\mu F$. Determine the period and frequency of oscillation. Define intrinsic standoff ratio.

Chapter.6 Voltage Regulators (16 marks)

3marks

20) Draw & explain zener diode as a voltage regulator.

21) Draw the pin diagram of 1. IC78XX 2. IC 79XX 3. IC LM723

4 marks

22) Draw & explain transistorized shunt regulator.

23) Draw the block diagram of DC power supply. Explain the function of each block.

24) Draw & explain transistorized series regulator.

25) Construct a dual power supply capable of giving $\pm 12V$ using 78XX and 79XX IC's.

26) State important features of IC 723. What is the use of CL and CS terminals?

27) For a zener diode voltage regulator , if $V_s= 20V$, $V_z= 10V$, $R_s=500\Omega$, $R_L = 1K\Omega$, find
a. Load voltage, b. Voltage drop across series resistor R_s and c. current through zener diode.

