

**Question Bank (G scheme)**

**Name of subject: LINEAR INTEGRATED CIRCUITS**

**Subject code: 17445**

**Semester :IV**

**Unit Test : I**

**Course : IS/IE/EJ**

**CHAPTER 1: OPERATIONAL AMPLIFIER(10 MARKS)**

**3 Marks :**

- 1) Define CMRR, Slew Rate, Gain Bandwidth Product
- 2) Define Input Offset voltage, Output Offset Voltage, PSRR.
- 3) Draw equivalent circuit and voltage transfer characteristics of an op-amp.

**4 Marks :**

- 4) Draw the block diagram of an op-amp and write the function of each block.
- 5) What is the use of level shifter stage? Draw its circuit diagram.
- 6) Write ideal and practical values of any four characteristics of an op –amp.
- 7) Assuming slew rate for 741 is 0.5 V/ $\mu$ sec. What is the maximum frequency of undistorted sine wave that can be obtained for a. 12V peak b. 2V peak

**CHAPTER 2: OP AMP CONFIGURATION(18 MARKS)**

**3 Marks :**

- 8) Distinguish open loop and close loop configuration. (6 pts.)
- 9) Describe the concept of virtual ground and virtual short.
- 10) Why open loop configuration is not used for linear applications?
- 11) Draw the unity gain amplifier. State any two applications of it.
- 12) Draw the input and output waveform of practical integrator and differentiator when the input is sine wave and square wave.
- 13) In an inverting amplifier let  $R_F = 100\text{ K}\Omega$  ,  $R_1 = 10\text{ K}\Omega$  and  $V_1 = 1\text{ V}$  calculate  
a. Input current b. Output Voltage c. Closed loop gain

**4 Marks Question:**

- 14) Draw the circuit diagram of close loop non- inverting amplifier and derive expression of its voltage gain.
- 15) Design the circuit to get output voltage  $V_o = 5\text{ V}$  and draw designed circuit.
- 16) It is desired to get an output using op-amp, given by the equation  $V_o = 5(V_1 - V_2) + 3V_3$

Design the circuit and draw the designed circuit.

- 17) Draw the circuit of closed loop difference amplifier using one op-amp. Derive the expression of its output voltage.
- 18) Draw the circuit diagram of basic integrator and practical integrator.

19) Draw the circuit diagram of basic differentiator and derive expression of its output voltage.

**CHAPTER 3: APPLICATIONS OF OP AMP(22 MARKS)**

**3 Marks:**

- 20) State the need of signal conditioning.
- 21) Draw and explain temperature compensated logarithmic amplifier using op-amp.
- 22) Draw the circuit diagram of I. A. using three op – amp and write its output equation.
- 23) Explain current to voltage converter. Write its applications.
- 24) Draw and explain Window detector.
- 25) Compare between Schmitt Trigger and Comparator.
- 26) Define UTP, LTP, Hysteresis with respect to Schmitt trigger

**4Marks :**

- 27) Draw the circuit of a V-I converter and derive an expression for the output current in terms of input voltage.
- 28) Draw the diagram of log amplifier using op-amp. Derive the expression for its output voltage.
- 29) Draw the sample and hold circuit using op-amp. Explain its working and show input and output waveform.
- 30) Draw the neat diagram of analog multiplier using log-antilog amplifiers and explain its operation.
- 31) Draw and explain zero crossing detector with i/p and o/p waveform.
- 32) Draw and explain Inverting Schmitt Trigger using IC 741.
- 33) With suitable circuit diagram explain Active peak detector.