

BHARATI VIDYAPEETH INSTITUTE OF TECHNOLOGY

Question Bank (K - Scheme)

Name of subject: Analog Electronics
Subject code: 313324

Unit Test :I
Course : EJ
Semester: III

Unit - I - Power Amplifiers (12 M)

2 Marks

1. List types of Power amplifiers.
2. Compare push pull and complementary symmetry amplifiers on the basis of
i) Type of transistors ii) Transformer required
3. Explain heat sink in power amplifier.
4. Define Gain and Distortion.

4 Marks

5. Draw and Explain class B push pull amplifier with input output waveforms.
6. Compare Class A, Class B, Class AB, and Class C
7. Class A power amplifier has an output power of 2W. If amplifier has an efficiency of 25%, then determine the total power drawn from the supply.

Unit – II- Op-amp and its Applications (18 M)

2 Marks

1. Define CMRR, Slew Rate.
2. Define Input Offset voltage, Output Offset Voltage.
3. Draw and label the symbol of OP-AMP.
4. Draw ideal and practical transfer characteristic of OP-AMP.
5. Draw labeled pin diagram of the symbol of OP-AMP IC 741
6. State ideal and practical value of given parameters of op-amp IC 741
(i) Input resistance (ii) Input offset current.
7. Draw labeled pin diagram of the symbol of OP-AMP IC 741.

4 Marks

8. Draw the block diagram of an op-amp and write the function of each block.
9. In closed loop inverting amplifier, $V_{in} = 1 \text{ Vp-p}$ sinewave at 1KHz, $R_1 = 470 \Omega$, $R_F = 4.7k\Omega$. Determine the value of output voltage V_o . Also sketch input and output voltage waveforms.
10. Describe the concept of virtual ground and virtual short.
11. Draw the closed loop circuit of OP-AMP with feedback in inverting mode. Give expression for output.
12. Draw the circuit diagram and output voltage relation for inverting summing amplifier.
13. Draw the circuit diagram of Op-Amp as a subtractor and write the equation for output voltage.
14. Compare Integrator and differentiator (any 4 points).
15. Draw the circuit diagram of basic integrator derive expression of its output voltage with its input and output waveforms.
16. Draw the circuit diagram of differentiator using Op-amp. Also draw input and output waveforms for i) sine wave ii) square wave
17. Draw the circuit of closed loop difference amplifier using one op-amp. Derive the expression of its output voltage
18. Draw the circuit of a V-I converter and derive an expression for the output current in terms of input voltage.
19. Explain current to voltage converter. Write its applications
20. Draw and Explain Schmitt trigger.
21. Draw and Explain Inverting Zero Crossing Detector with neat waveforms.
22. Draw and explain sample and hold circuit.

Unit – III - Waveform Generators (14 M)

2 Marks

1. Define feedback amplifier. State types of feedback.
2. Compare oscillator and amplifier on the basis of
 - i) Type of feedback
 - ii) Need of input signal.

4 Marks

3. List the types of feedback connection. Draw any one connection diagram.
4. Compare positive feedback and negative feedback.