

## QUESTION BANK (K Scheme)

Name of subject: Digital Electronics and Microcontrollers Applications

Course Title: DEM (314324)

Semester: 4K

Unit Test: I

Program Code: EE

### CHAPTER 1: Logic Gates and logic families (16 marks) (CO1) 13.71 (4+4+2+2+2)

#### 2 marks

1. Perform the following Conversion:

a)  $(110101)_2 = ( \quad )_{10}$

b)  $(A4)_{16} = ( \quad )_{10}$

c)  $(247)_{10} = ( \quad )_8$

d)  $(A72)_{16} = ( \quad )_8$

e)  $(736)_8 = ( \quad )_2$

f)  $(2F9)_{16} = ( \quad )_2$

g)  $(123)_8 = ( \quad )_{16}$

h)  $(95)_{10} = ( \quad )_{16}$

2. Sketch the symbol of EX- OR and EX- NOR gate with its truth table.

3. Identify the following IC and draw the pin diagram of any one IC – 7400 and 7402.

4. Why NAND and NOR are said to be universal gates?

#### 4 marks

5. Explain switch circuit of NAND & NOR gate with Truth table.

6. Identify the following IC and draw its symbol & truth table (Basic Gates).

7. Construct basic gates using universal gates.

8. Add  $(569)_{10}$  &  $(687)_{10}$  in BCD.

9. Perform the subtraction using  $(45)_{10} - (47)_{10}$  using

a) 1's Complement method

b) 2's Complement method

10. Draw circuit diagram of the following with truth table:

a) Half Adder

b) Half Subtractor

c) Full Adder

d) Full Subtractor

## **CHAPTER 2: Digital Logic Circuits (14 marks) (CO2) 12 (4+4+2+2)**

### **2 marks**

11. Define multiplexer & state its necessity.
12. Write the excitation table for SR FF, JK-FF, T-FF and D-FF.
13. Define modulus of a counter? Write down the number of flip flops required for mod-5 counter?
14. Differentiate between MUX & DEMUX. (4 points)
15. Compare synchronous & asynchronous counter. (4 points)

### **4 marks**

16. Draw Block diagram of 8:1 Multiplexer and write its truth table.
17. Design 1: 16 demultiplexer using 1: 4 demultiplexers.
18. Draw clocked SR flip flop. State the use of preset and clear in flip flop.
19. Compare all flip-flops on the basis of logic diagram, circuit diagram and truth table.
20. Draw circuit diagram & truth table of 4-bit asynchronous counter.

## **CHAPTER 3: 8051 Microcontroller Architecture (08 marks) (CO3) 6.85 (4+2)**

### **2 marks**

21. State the different type of buses.
22. Define: (i) Address bus (ii) Data bus (iii) Control bus.
23. Define microcomputer & microcontroller

### **4 marks**

24. Compare microcomputer & microcontroller. (Any four points).
25. List any eight features of microcontroller 8051.
26. Compare Harvard and Von-Neuman architecture. (definition, diagram, applications, physical address )